

PX2505 - Electronics Lab Report - Haunted Doll Factory

PX2505 - Electronics Lab Report - Haunted Doll Factory

**Sidney Pauly
52104132
March 17, 2023**

Declaration

I certify that this report has been written by myself, except where otherwise indicated

University of Aberdeen
Scotland
UK

<https://github.com/sidney-pauly/papers>

Contents

1	Introduction	1
2	Experiment	1
2.1	Aim	1
2.2	Theory	2
2.3	Verifying the theory	4
2.4	Schematic Diagram	4
2.4.1	Input	5
2.4.2	Logic	5
2.4.3	Output	5
2.5	The Physical Circuit	6
2.5.1	Components	6
2.5.2	Input	7
2.5.3	Logic	7
2.5.4	Output	7
2.6	Result	7
3	Conclusion	9

1 Introduction

The electronics section of the PX2505 course focuses on digital logic or TTL (Transistor-transistor logic). Broadly speaking the aim of digital logic is to perform logic operations to perform various practical tasks. The most simple case is to directly evaluate logical conditions electronically. An example could be a traffic light assembly: The light for the pedestrians should only be set to green if the request button is pressed and no car is currently on the intersection, but not if it was already green in the last 30s. Those conditions can be translated into formal logic and further into a digital circuit which then performs these operations. In principle digital logic circuits can execute any higher order algorithms, which is what computers do, However this experiment only focuses on simple logic like in the example. The aim will be to analyze the requirements set out, build a schematic version of the circuit and finally a physical working version of the same.

The "Haunted Doll Factory" is exactly about such an application of basic logic. The doll has four inputs and four outputs and the task is to have the motors (outputs) only turn on when specific inputs are active. Using simple logic gates (AND, OR, XOR, etc.) these requirements can be implemented both as an actual circuit as well as a simulation one (with the Multisim simulation tool)

A further practical goal when building digital circuits is to achieve the requirements with as little components as possible. This is because fewer components reduce the amount of failure points as well as the energy consumption of the device. To reduce the amount of components while still achieving the same logical behavior analytical methods can be used. Boolean algebra is a mathematical description of logic and can therefore be used to manipulate logical statements and to reduce them to their simplest form. This technique was used in this experiment to greatly reduce the number of required logic gates.

2 Experiment

2.1 Aim

The Lab Manual[1] sets out the following scenario: We are tasked with designing an electronic circuit, that controls the behavior of a (haunted) doll. The doll has four inputs (those could be buttons or switches) and four outputs (motors that can either be turned on or off). The desired logical behavior of how these inputs and outputs are related is given by (Table 1):

INPUT				OUTPUT			
S_1	S_2	S_3	S_4	M_1	M_2	M_3	M_4
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	1
1	0	1	0	1	0	1	0
1	0	1	1	0	0	0	0
1	1	0	0	1	1	0	0
1	1	0	1	0	0	0	0
1	1	1	0	1	1	1	0
1	1	1	1	0	0	0	0

Table 1: Desired Behavior of the Doll [1]

S_{1-4} specify the four inputs, while M_{1-4} specify the four outputs (motors). If a given input shows 0 its off, if it shows 1 its on, the same applies to the motors.

2.2 Theory

At first glance the behavior of the doll looks quite complex. It is not immediately clear what sort of simple logical expression could describe the behavior of the doll in its entirety. Luckily there are tools to analyze such requirements and thus arrive at a simplified expression.

The first thing that could be asked is for what inputs a motor is on? This can then be translated into logical language and those logical expression can then be reduced. A simple example is Motor 2, it is on if input 1 is on, input 2 is on, input 3 is off and input 4 is off. Alternatively it is also on if input 1 is on, input 2 is on, input 3 is on and input 4 is off. For all other cases the motor is off. This can also be represented in boolean algebra:

$$M_2 = (S_1 * S_2 * \bar{S}_3 * \bar{S}_4) + (S_1 * S_2 * S_3 * \bar{S}_4)$$

Translated to natural language multiplication means "and", addition "or" and a bar over the respective value means "not". The nice thing about this representation is that relevant algebraic rules hold, i.e. transitivity, commutativity, etc.[1].

Thus the above expression can be simplified to:

$$M_2 = (S_1 * S_2 * \bar{S}_4)(S_3 + \bar{S}_3)$$

as something OR not something ($X + \bar{X}$) is always true the expression further simplifies to:

$$M_2 = S_1 * S_2 * \bar{S}_4$$

Through the same technique similar expressions for the other motors could be derived. Then the expressions could be compared and similar operations could then be implemented with the same physical components to reduce their overall count.

However in case of the doll there is a quicker and more effective way: converting the binary input and output signals to decimal. As we are more used to decimal (and because decimal represents more information in fewer digits) it is sometimes more intuitive to understand and to infer patterns. Table 2 shows such a decimal translation. The representation treats every input as a digit of a four digit binary number. The same is done for the output.

Input	Active Motor	Output
0		0
1	M_4	1
2	M_3	2
3		0
4		0
5		0
6		0
7		0
8	M_1	8
9	M_1, M_4	9
10	M_1, M_3	10
11		0
12	M_1, M_2	12
13		0
14	M_1, M_2, M_3	14
15		0

Table 2: The behavior translated to Decimal

Doing this translation immediately makes it obvious that there are just two cases:

1. The output is 0 (all motors are off)
2. The input is the same as the output (the motors belonging to the respective input are on)

The result of this realization is that the task can be rephrased: we need a circuit that is only on for the binary representations of the numbers 1, 2, 8, 9, 10, 12 and 14. The most direct (but also most inflated) boolean representation of the same is this:

$$F = (\bar{S}_1 \bar{S}_2 \bar{S}_3 S_4) + (\bar{S}_1 \bar{S}_2 S_3 \bar{S}_4) + (\bar{S}_1 S_2 \bar{S}_3 \bar{S}_4) + (S_1 \bar{S}_2 S_3 S_4) + (S_1 \bar{S}_2 S_3 \bar{S}_4) + (S_1 S_2 \bar{S}_3 \bar{S}_4) + (S_1 S_2 S_3 \bar{S}_4)$$

Through a lot of algebraic manipulation one can end up with the following expression:

$$F = S_1 \bar{S}_4 + \bar{S}_2 S_3 \bar{S}_4 + \bar{S}_2 \bar{S}_3 S_4$$

This expression can be further simplified by using the fact that $X\bar{Y} + \bar{X}Y = X \oplus Y$, i.e. X and not Y or not X and Y is the same as only X or only Y (exclusive OR):

$$F = S_1 \bar{S}_4 + \bar{S}_2 (S_3 \oplus S_4) \tag{1}$$

This simple expression now distinguishes the two cases laid out previously. If the expression is false, no motors should be on. If it is true the motors which have their corresponding input on should be on. Algebraically this can be expressed as

$$M_n = S_n F \tag{2}$$

Note that this expression basically acts as a filter or mask on the inputs. Because of this the expression will from now on be referred to as the logic filter.

2.3 Verifying the theory

Before spending a lot of time on building circuits it is useful to know that the discovered logic expression does indeed recover the desired logical behavior. The following script runs through all different input combinations and applies the logical expression to them. The result is then printed out.

```
1 import pandas as pd
2
3 result = [0] * 16
4
5 for i in range(0, 16):
6
7     # Decimal to binary digit conversion
8     s_1 = (8 & i) > 0
9     s_2 = (4 & i) > 0
10    s_3 = (2 & i) > 0
11    s_4 = (1 & i) > 0
12
13    # Calculate the logic filter
14    F = (s_1 and not s_4) or (not s_2 and (s_3 ^ s_4))
15
16    # Apply the filters to the input and thus produce the output
17    result[i] = [s_1, s_2, s_3, s_4, F and s_1, F and s_2, F and s_3, F and s_4]
18
19 # Print the result through a pandas data frame to have it formatted
20 print(pd.DataFrame(result))
```

The output of this script matches table 1 exactly, confirming that the simplification process worked

2.4 Schematic Diagram

The first step is to draw a schematic diagram of the resulting circuit. The following schematic diagram was drawn and then simulated with Multisim:

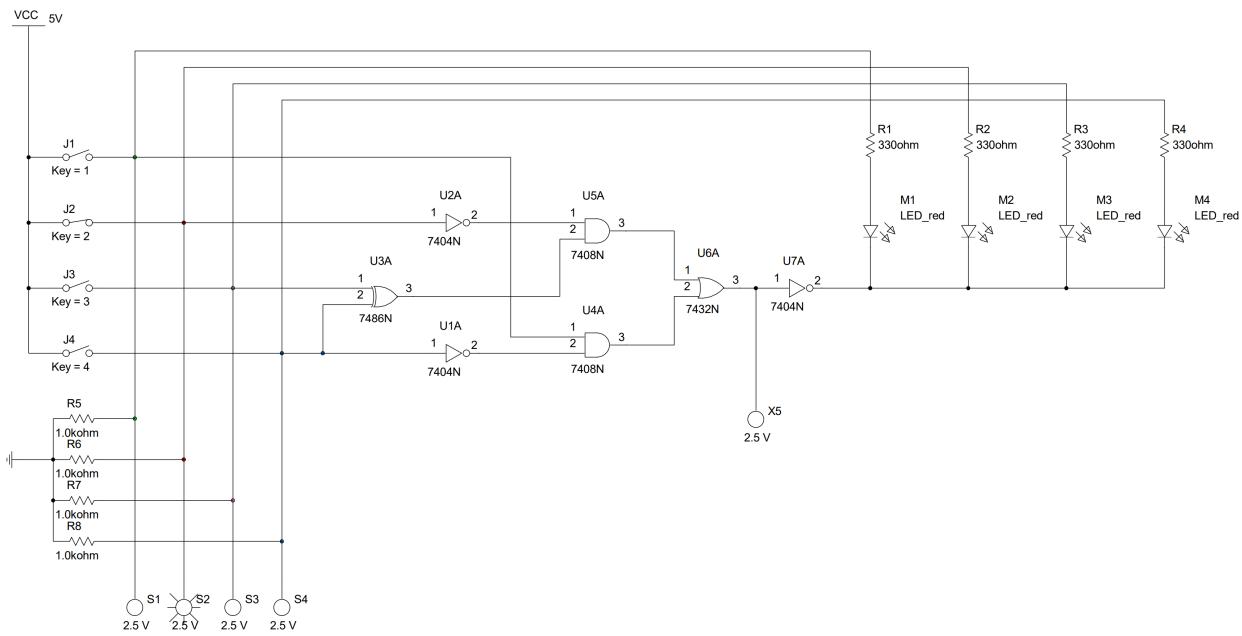


Figure 1: Schematic diagram of the "Haunted Doll" circuit

The resulting circuit consists of three main sections. Each section has some additional features and optimizations. Because the circuit is designed with the multi sim software it can be simulated. The circuit showcased in figure 1 was tested for all possible inputs of S_{1-4} and yielded the behavior expressed in table 1.

2.4.1 Input

The input section consists of four switches. Each of the switches corresponds to one of the inputs S_{1-4} . In the diagram they are labeled with J1-J4. If the input switches are closed the corresponding wire will be at VCC voltage (5V). This voltage (also referred to as HIGH) corresponds to an input value of 1. A value of 0 is represented by 0V (also called GND). Note that the input wires are always connected to GND through a $1k\Omega$ resistor. This connection ensures that when the input switches are open that the input wire is at a valid logic value of GND. If there would be no connection in that case the corresponding input would have an undefined value, which could lead to undefined behavior. Connecting the input through a $1k\Omega$ resistor ensures that in case the switch is closed the input will be at VCC voltage, as the wire without resistance "overpowers" the connection with resistor.

In the schematic additional logic probe indicator lights are attached to the input cables (S1-S4). Their purpose is to quickly and easily determine the state of the given input.

2.4.2 Logic

The logic section takes in the four input signals and processes them. The implemented logic corresponds exactly to the logic filter F (equation 1). The logic section ends at the logic probe indicator light (label X5). This light is there to quickly determine the value of F (the logic filter value). The subsequent inverter (label U7A) is not considered part of that section. It belongs to the output section and its purpose will be explained subsequently.

To implement equation 1 the corresponding 74xx series TTL logic components are used:

1. 7404N Inverter (NOT)
2. 7486N XOR
3. 7408N AND
4. 7432N OR

The layout corresponds to the equation 1:1. This can be seen easiest going backwards from the OR gate (label U6A). Its lower input corresponds to the left component of equation 1 and its upper input to the right component. Consequently the lower AND gate (label U4A) has S_1 and \bar{S}_4 as inputs (S_4 gets inverted through inverter U1A). Equally the upper AND gate (label U5A) is connected to \bar{S}_1 (inverter U2A) and the exclusive or gate (label U3A) that combines S_3 and S_4 .

2.4.3 Output

The last section is the output section. It has two tasks, display the result through LEDs (M_{1-4} standing in for the motors) as well as applying the logic filter F to the inputs S_{1-4} (Equation 2). The obvious way to do the later would be to add another four AND gates combining F and S_n . Instead another trick can be employed here. Because the LEDs are diodes they are only on if they are connected to HIGH on one side (Anode A) and to LOW on the other (Cathode K). In any other configuration the LEDs won't turn on. This behavior can be abused as the LED therefore acts as an AND gate with the equation $O = A\bar{K}$. To emulate the behavior of equation 2 the filter F simply has to be inverted and connected to the Cathodes (K) (this is why the inverter with label U7A is needed) and the inputs S_n to each of the anodes.

To prevent the LEDs from overheating 330Ω current limiting resistors are added in series.

2.5 The Physical Circuit

The implemented physical circuit is the direct implementation of the schematic, with some minor modifications for practicality.

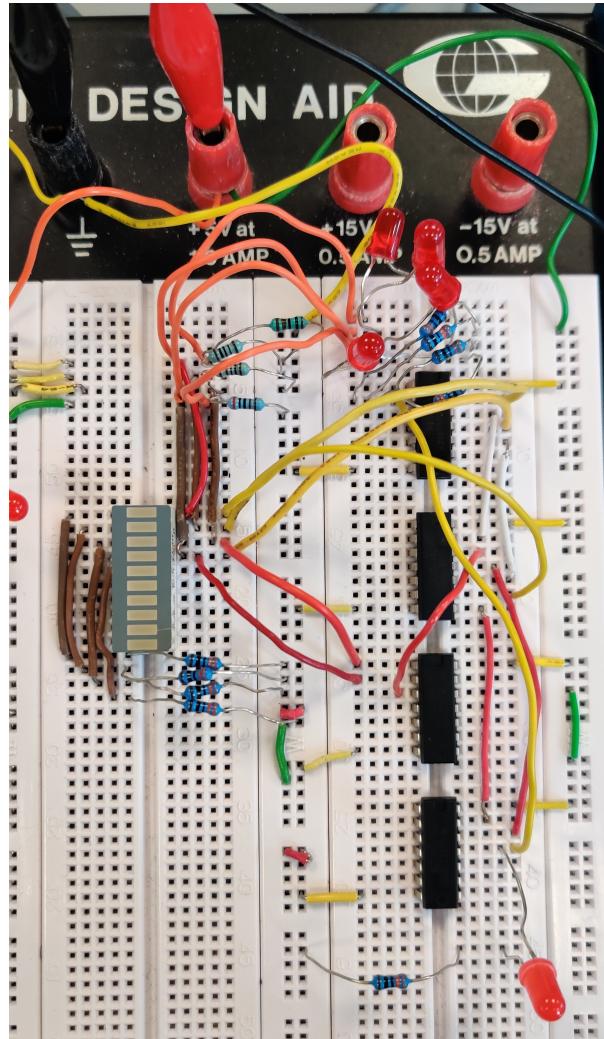


Figure 2: The physical "Haunted Doll" circuit

2.5.1 Components

The following components were used in the circuit:

1. 1 8-digit LED bar
2. 5 Red LEDs
3. 9 330Ω resistors
4. 4 $1k\Omega$ resistors
5. 1 Texas Instruments S7404 Inverter chip[2]
6. 1 Texas Instruments SN74HC86 XOR chip[3]
7. 1 Texas Instruments SN74HC32 OR chip[4]
8. 1 Texas Instruments SN74LS08 AND chip[5]

Just like the schematic the physical circuit consists of the same three sections.

2.5.2 Input

The input section covers the left breadboard (Figure 2). The input section consist of an 8-digit LED bar which shows which of the inputs are currently HIGH. From top to bottom the first four LEDs thus indicate the state of S_1 to S_4 . The cathode pins of the LEDs are connected to ground through 330Ω resistors to prevent them from overheating (4 dark blue resistors below the LED bar). The anodes of the LED bar are connected to ground through $1k\Omega$ resistors, to pull them LOW in the default case. Additionally 8 pins jumper pins are layed out, four of them connected to VCC the other four leading to the respective inputs S_{1-4} . Jumper wires can be inserted here, which act as the switches.

2.5.3 Logic

The logic section is on the right breadboard in figure 2. It consists of the four logic chips. From to bottom those are the Inverter chip, the AND chip, the OR chip and the XOR chip. The chips are then wired up as layed out in the schematic (figure 1). The respective pin layout was taken from the referenced texas instruments data sheets. The bottom LED indicates the status of the logic filter and lights up when the later is outputting HIGH.

2.5.4 Output

Just like in the schematic the output consists of four LED indicator lights. From top to bottom they indicate if the motors of the doll (M_1 to M_4) are on. Their cathodes connect to the inverted signal of the logic filter and their anodes to the inputs S_{1-4} . Again all LEDs are connected in serial through 330Ω resistors.

2.6 Result

The circuit works as expected this is showcased by the following to images (one for each case):

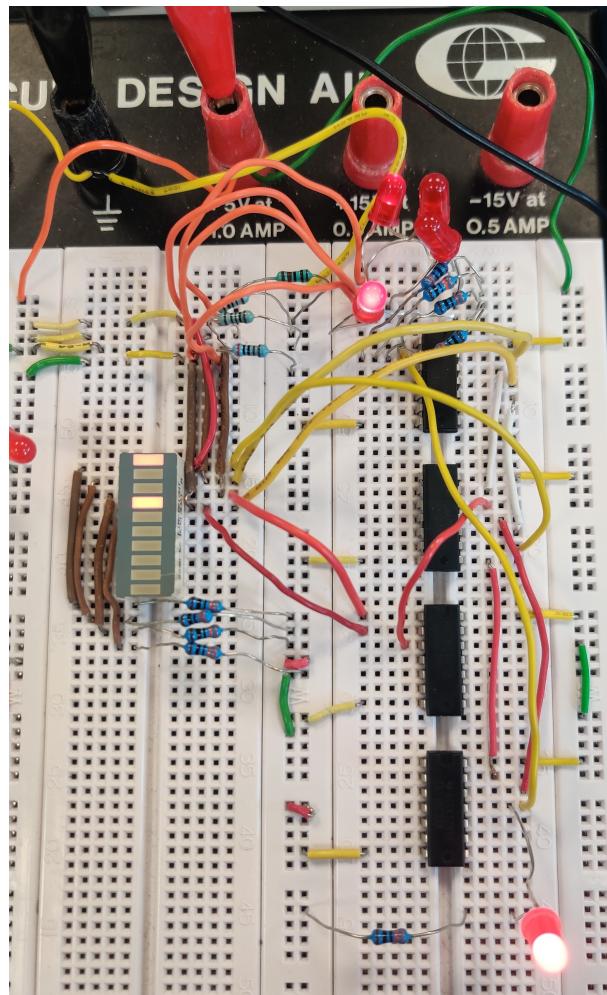


Figure 3: Input 1001 (Decimal 9) - Logic filter and motors M_1/M_4 are on

In figure 3 the inputs S_1 and S_4 are on. This corresponds to a the binary number 1001 or decimal 9. Looking at table 2 for input 9 motors M_1 and M_4 should be on. Exactly this can be seen: the LEDs corresponding to those motors light up correctly. Additionally the filter indicator LED is also lighting up showing that the logic section correctly determined the filter condition.

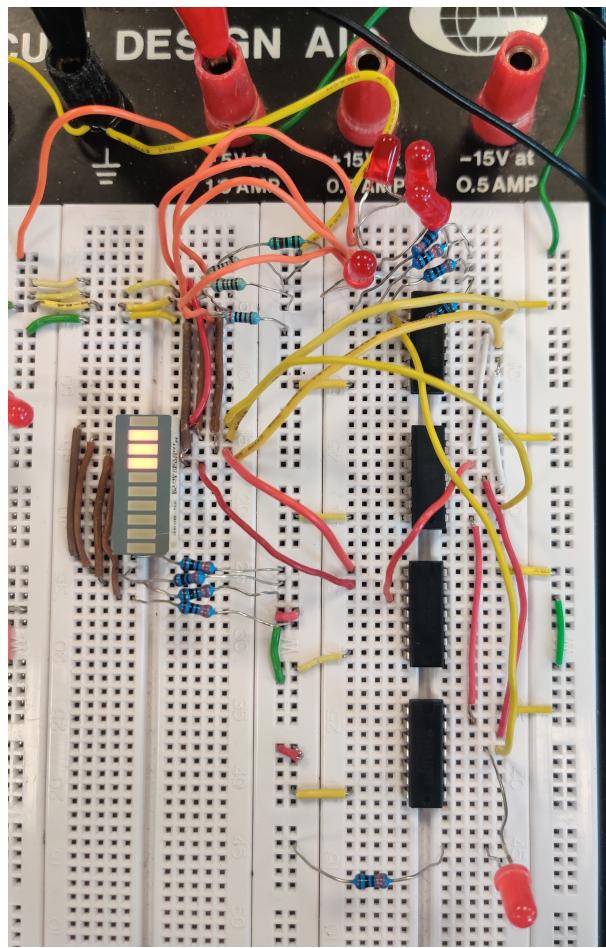


Figure 4: Input 0111 (Decimal 7) - Logic filter and motors are off

Figure 4 shows one of the cases where the logic filter is LOW. Inputs S_2 , S_3 and S_4 are on. This corresponds to the binary number 0111 or decimal 7. Looking at table 2 for input 7 no motors should be on. This is what can be seen in the physical circuit, even though the inputs for motors M_{2-4} are HIGH the LEDs don't light up. This is because the logic filter correctly outputs LOW, thus disabling all LEDs as both cathode and anode are HIGH (remember that the logic filter signal gets inverted).

The circuit shows the correct behavior for all 16 different input cases. Images showing all other cases are attached to the report.

3 Conclusion

The provided materials and components were suitable to implement and optimize a logical circuit given specific behavior requirements. To minimize the number of components and therefore the complexity of the final design the boolean algebra simplifications outlined in the lab manual[1] were very effective. The usage of Multisim to model the circuit were both effective to flesh out a design and to verify that it was working before actually implementing it. Especially because of this the set time frame for the experiment was adequate.

References

1. Mcphearson DR. PX2505 Practical Optics & Electronics Electronics Manual. University of Aberdeen
2. SN5505, SN54LS04, SN54S04, SN7404, SN74LS04, SN74S04, SN74S04 Hex Inverters. SDLS029C. Texas Instruments Incorporated. 2004 Jan. Available from: https://www.ti.com/lit/ds/symlink/sn7404.pdf?ts=1679056847689&ref_url=https%253A%252F%252Fwww.google.com%252F [Accessed on: 2023 Mar 17]

3. SNx4HC86 Quadruple 2-Input XOR Gates. SCLS100F. Texas Instruments Incorporated. 2021 Apr. Available from: <https://www.ti.com/product/SN74HC86te> [Accessed on: 2023 Mar 17]
4. SNx4HC32 Quadruple 2-Input OR Gates. SCLS200F. Texas Instruments Incorporated. 2021 Apr. Available from: https://www.ti.com/lit/ds/symlink/sn74hc32.pdf?ts=1679088242595&ref_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FSN74HC32 [Accessed on: 2023 Mar 17]
5. SN5408, SN54LS08, SN54S08, SN7408, SN74LS08, SN74S08 QUADRUPLE 2-INPUT POSITIVE-AND GATES. SDLS033. Texas Instruments Incorporated. 1988 May. Available from: https://www.ti.com/lit/ds/symlink/sn74ls08.pdf?ts=1679022560845&ref_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FSN74LS08%253Futm_source%253Dgoogle%2526utm_medium%253Dcpc%2526utm_campaign%253Dasc-int-null-prodfolddynamic-cpc-pf-google-wwe_int%2526utm_content%253Dprodfolddynamic%2526ds_k%253DDYNAMIC%2BSEARCH%2BADS%2526DCM%253Dyes%2526gcls%253Dds%2526gcls%253Dds [Accessed on: 2023 Mar 17]